



# Microprocessors

TE 258

WEEK 2: BASIC COMPUTER ORGANIZATION






# Microprocessors & Microcontrollers





# Basic Computer Organization

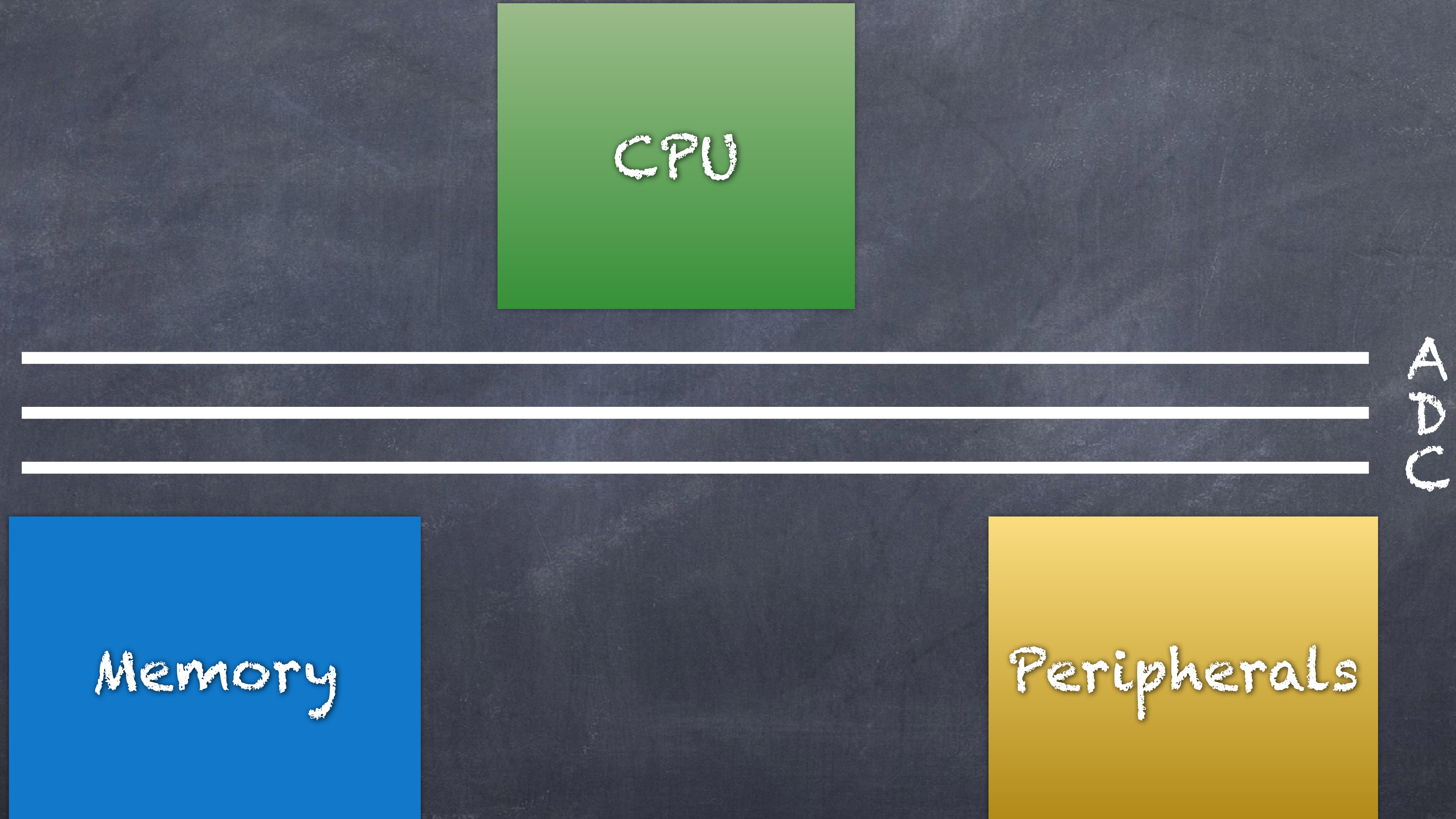





# Memory Interfacing Problem

## Example (Design):

Consider a CPU with a 16 bit address bus and an 8-bit data bus.

How do you interface 8 memory chips (2K x 4 bit) with it?





# Memory







# Memory

Address  
Bus



CS



Data  
Bus



Read  
 $\overline{RD}$

Write  
 $\overline{WR}$





# Memory Interfacing: ROM & RAM

## Example (Design):

8KB ROM, 16KB RAM.

CPU  $\Rightarrow$  16 bit Address Bus, 8 bit Data Bus.

ROM Starting Address = 0000H

RAM Starting Address = 8000H

ROM/RAM Size = 4KB x 8 bit





# Register

Parallel Input



Serial  
Input




n-bit






# Register

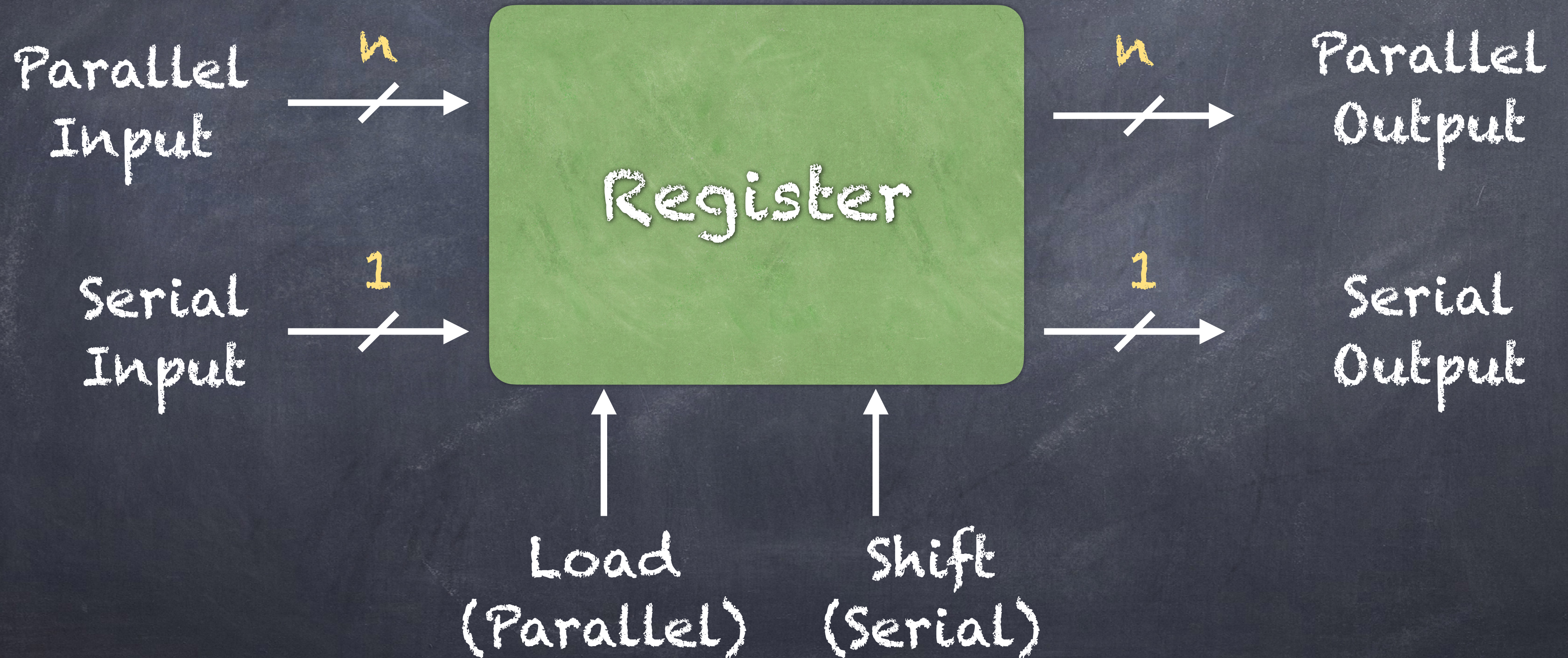





# Processor Internals

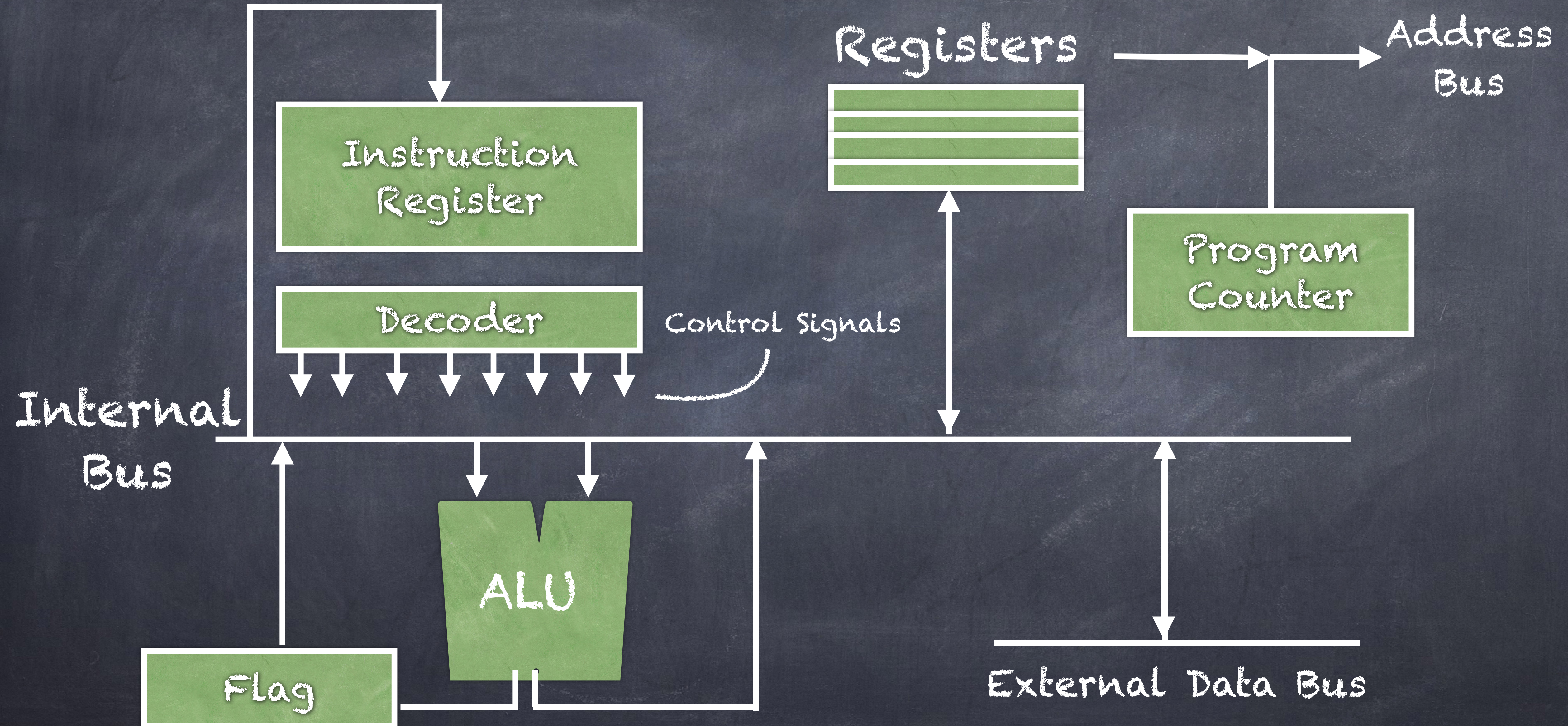







# Processor Internals

How the Control Part works

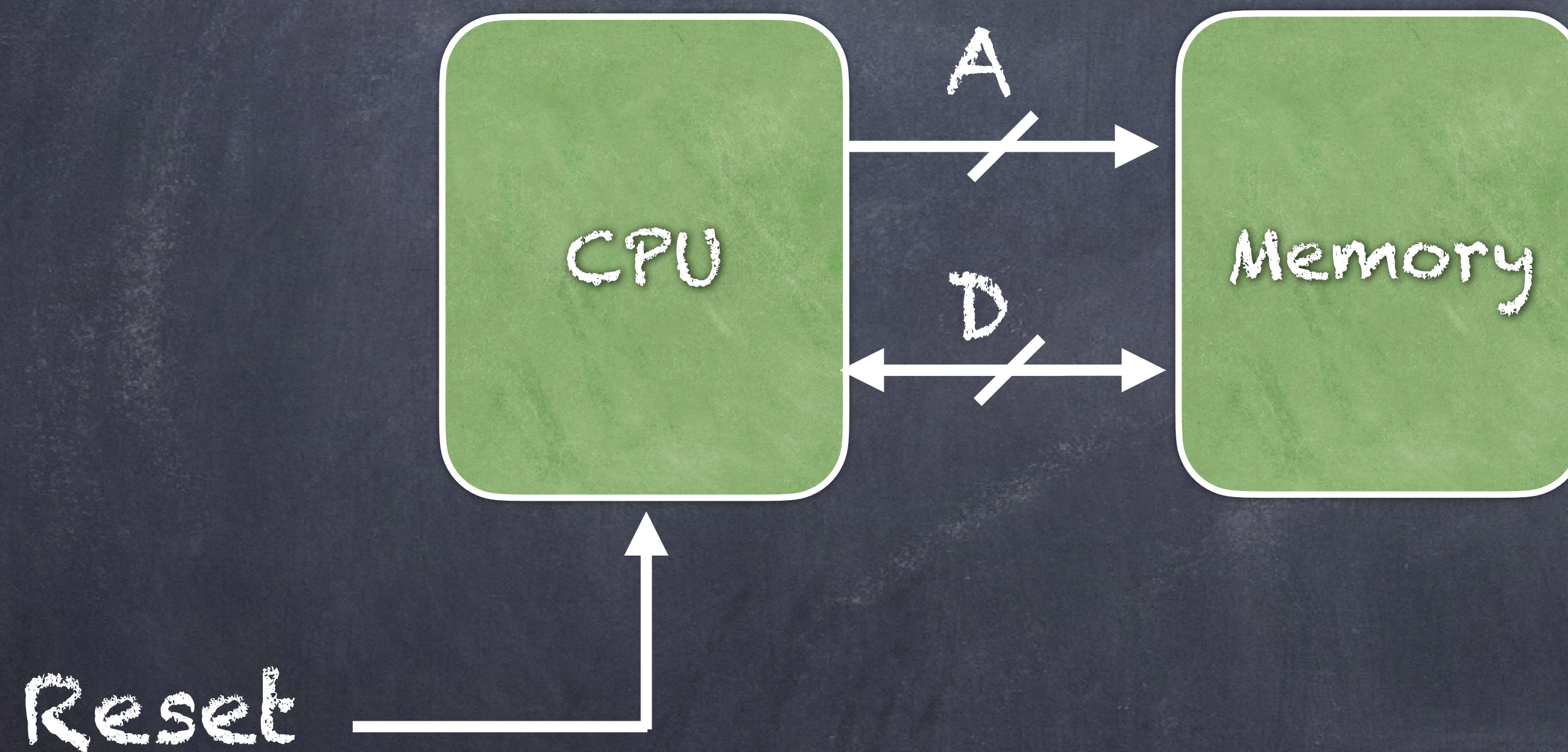

CPU Execution Cycle

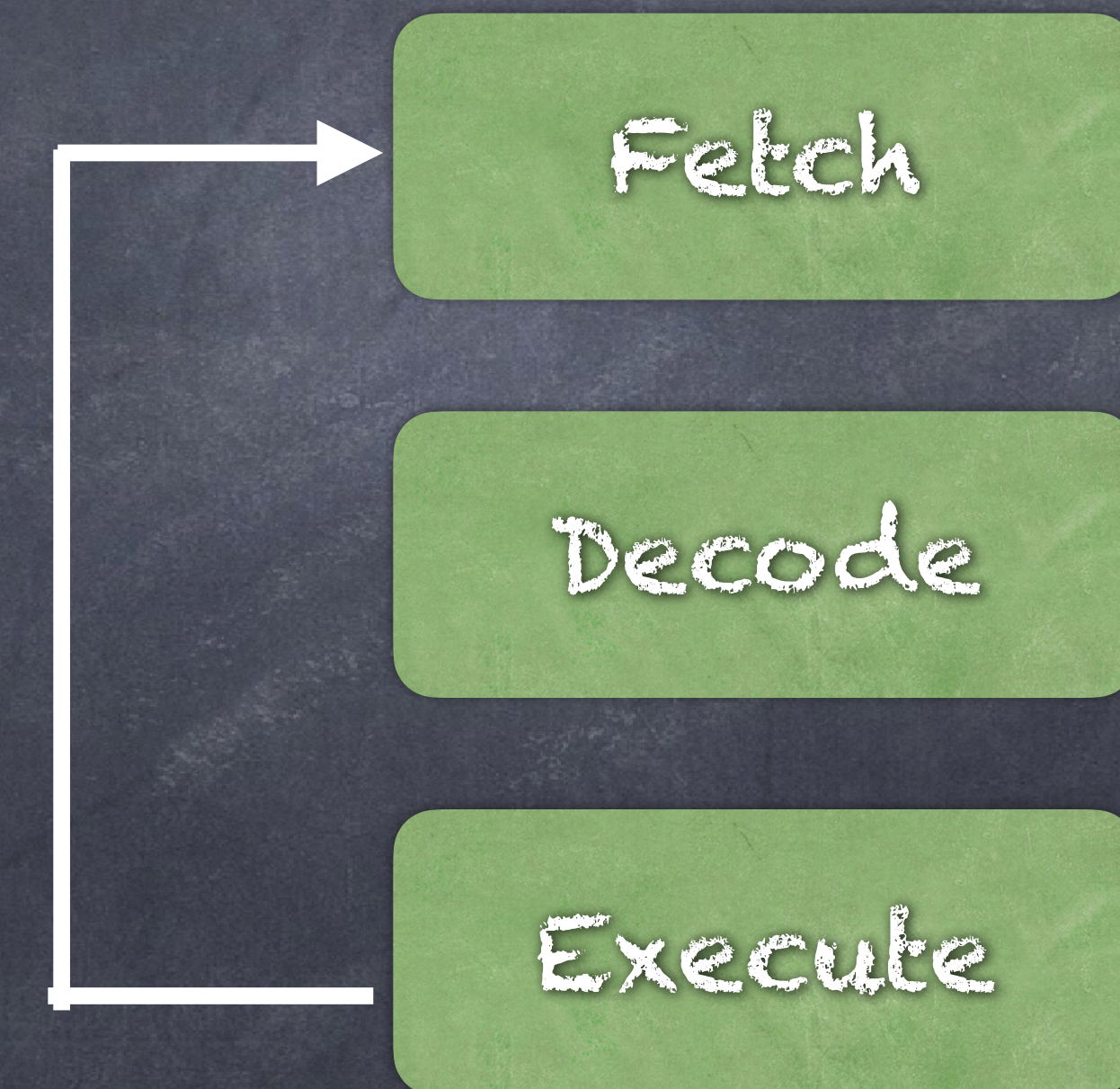






# Processor Internals

Example:

1. LOAD R0, 1000

2. ADD R0, R1, R2

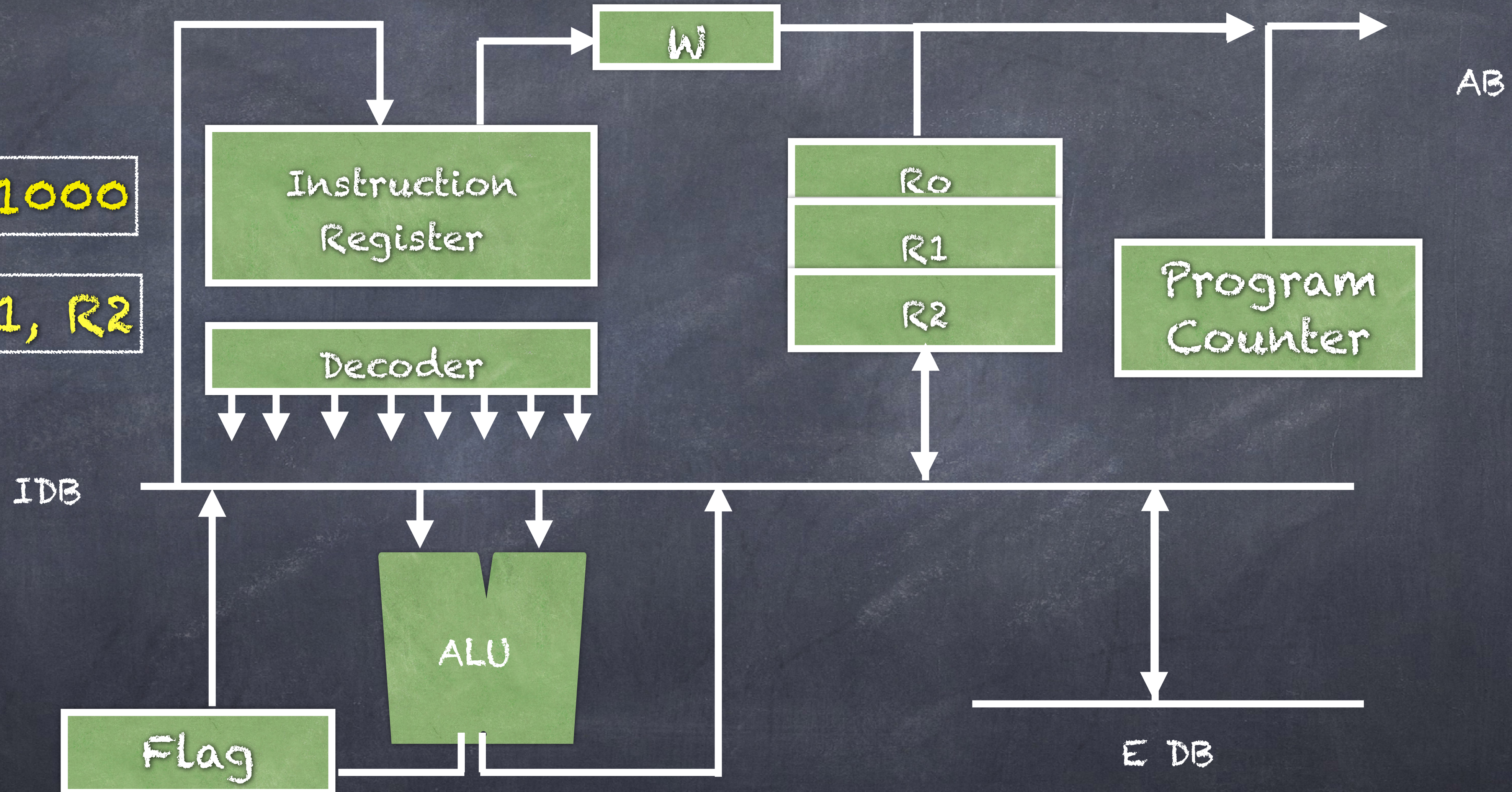





# Processor Internals

Example: **LOAD R0, 1000**

T1: Enable PC, Memory RD

T2: Load IR

T3: Decode, Increment PC

T4: Load W, Enable IR

T5: Enable W, Memory RD, Load R0





# Processor Internals

Example:

ADD R0, R1, R2

T1: Enable PC, Memory RD

T2: Load IR

T3: Decode, Increment PC

T4: Enable R0, Enable R1, ADD ALU, Load R2





# 8085 MICROPROCESSOR





Next...

- 8085 Microprocessor